

CSCE-312 QUIZ2 – TOTAL 15PTS

CSCE-312 | MONDAY FEB 8, 2016


NAME: JIAYI HUANG

UIN:

1. [5pts] Assuming AND gates have a delay of 2 ns, OR gates have a delay of 1 ns, and XOR gates have a delay of 3 ns, compute the longest time required to add two numbers using an 8-bit carry-ripple adder. (or 8 full adders) (either) 2'

An 8-bit carry-ripple adder contains 7 full adders and 1 half adder. Both the FA and HA have a maximum gate delay of 3 ns. Therefore, 8 adders \times 3 ns/adder = 24 ns¹ is required for an 8-bit carry ripple adder to ensure a correct sum is on the adder's output. (An Answer of 23 ns is also acceptable since the carry out of a half-adder will be correct after 2ns, not 3ns, and a half-adder may be used for adding the first pair of bits

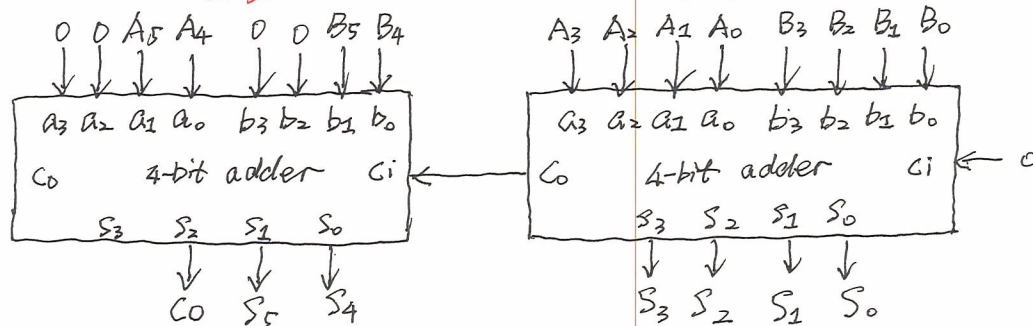2. [5pts] Design a system that computes the sum of two 6-bit numbers using 4-bit carry- ripple adders. Hint: Use cascading of the carry-ripple adders to build the sum of three 8-bit adders. 2.5'



3. [5 pts, 1pt each] Convert the following decimal numbers to 8-bit two's complement binary form:

- a. 4 0 0 0 0 0 1 0 0
- b. -2 1 1 1 1 1 1 1 0
- c. -25 1 1 1 0 0 1 1 1
- d. -128 1 0 0 0 0 0 0 0
- e. 126 0 1 1 1 1 1 1 0